

B.Tech. Degree II Semester Regular Examination July 2024**CE/ME/SE 23-200-0205A BASIC ELECTRONICS ENGINEERING***(2023 Scheme)*

Time: 3 Hours

Maximum Marks: 50

Course Outcomes

On successful completion of the course, the students will be able to:

CO1: Illustrate the concept of diode in rectifiers, filter circuits and wave shaping.

CO2: Interpret the functioning of oscillators and operational amplifiers.

CO3: Explain the principle of embedded systems and sensors.

CO4: Summarise the functioning of a communication system and different modulation technologies.

Bloom's Taxonomy Levels (BL): L1 – Remember, L2 – Understand, L3 – Apply, L4 – Analyze, L5 – Evaluate, L6 – Create

PO – Programme Outcome

PART A

(Answer ALL questions)

	(5 × 2 = 10)	Marks	BL	CO	PO
I. (a) What is meant by doping? How are p-type semiconductors formed?	2	2	L2	1	1
(b) An operational amplifier with a negative feedback applied produces an output of 2.5 V when an input of 5.5 mV is present. Determine the closed-loop voltage gain.	2	2	L5	2	1,5
(c) Differentiate RISC and CISC processors.	2	2	L1	3	1
(d) Differentiate HLR and VLR in GSM architecture of mobile communication.	2	2	L2	4	1
(e) List out the reasons for, choosing the downlink frequency lower than that of the uplink frequency in satellite communication.	2	2	L2	4	1

PART B

(4 × 10 = 40)

II. (a) Explain the working of a full wave bridge rectifier using filter with circuit diagram and relevant input, output waveforms.	7	7	L3	1	1,5,12
(b) An amplifier produces an output voltage of 8 V for an input of 100 mV. If the input and output currents in this conditions are 8 mA and 200 mA respectively, determine the voltage gain, current gain and power gain of the amplifier.	3	3	L3	1	1,5,12
OR					
III. (a) What do you mean by multistage amplifiers? Explain the working of a two stage RC coupled amplifier with a neat circuit diagram.	6	6	L3	1	1,5,12
(b) Discuss the need of voltage regulators in power supply systems with necessary circuit diagram.	4	4	L3	1	1,5,12
OR					
IV. (a) Explain the inverting and non-inverting configurations of an op-amp. List out the ideal op-amp characteristics.	7	7	L2	2	1,5,12
(b) Implement the EX-NOR function using basic gates.	3	3	L3	2	1,5,12
OR					
V. (a) Explain the working of a Ladder network oscillator using BJT with a neat circuit diagram.	7	7	L3	2	1,5,12
(b) Define CMRR and slew rate of an op-amp with typical values.	3	3	L2	2	2

(P.T.O.)

BTS-II(R)-07-24-2831

		Marks	BL	CO	PO
VI	(a) With a block diagram briefly describe the elements of an embedded system and explain about the core in detail.	7	L2	3	1,5,12
	(b) What are the differences between a microprocessor and a microcontroller?	3	L2	3	1,5,12
OR					
VII.	(a) Explain the working of a 7-segment LED display with suitable diagrams and examples. Discuss the two types of configurations with necessary diagrams.	7	L2	3	1,5
	(b) What are transducers? Differentiate sensors and actuators used in an embedded system with suitable examples.	3	L2	3	1
VIII.	(a) Explain in detail the working of an optical communication system with a neat schematic diagram. Mention any two advantages and disadvantages.	7	L4	4	1,5
	(b) What do you mean by multiplexing? Differentiate TDM and FDM with suitable examples.	3	L2	4	1,5,12
OR					
IX.	(a) Define modulation and briefly explain AM and FM with necessary diagrams.	5	L2	4	1,5,12
	(b) Define satellite communication and briefly explain the working of earth station transmitter employed in the satellite communication with necessary block diagrams.	5	L3	4	1,5,12

Bloom's Taxonomy Levels

L1 - 5%, L2 - 50%, L3 - 30%, L4 - 5%, L5 - 10%.
