

**B.Tech. Degree I Semester Regular and Supplementary/
II Semester Supplementary Examination November 2018**

CS/EC/IT GE 15-1104 B & CE/EE/ME/SE GE 15-1204 A
BASIC ELECTRICAL ENGINEERING
(2015 Scheme)


Time : 3 Hours

Maximum Marks : 60


PART A
(Answer *ALL* questions)

(10 × 2 = 20)

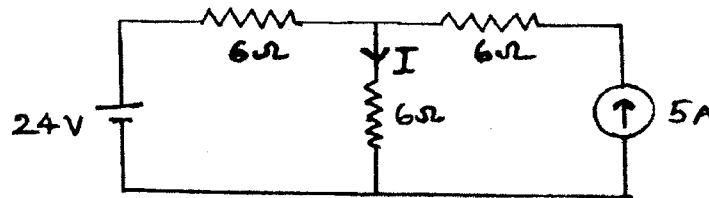- I. (a) State Norton's theorem.
(b) Derive an expression for the energy stored in a capacitor of 'C' Farads when charged to a potential difference of 'V' volts.
(c) Calculate the current 'I' in the network using mesh analysis.



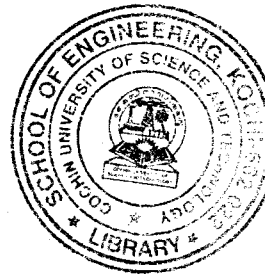- (d) Compare electric and magnetic circuits.
(e) Explain Faraday's law of electromagnetic induction and Lenz's Law.
(f) The voltage across and current through a circuit are given by
 $v = 250 \sin(314t - 10^\circ)$; $i = 10 \sin(314t + 50^\circ)$
Calculate the impedance, resistance and reactance of the circuit.
(g) Prove that in a purely inductive circuit the current lags behind the voltage by an angle of 90° and the average power consumed is zero.
(h) Explain the advantages of three phase system compared to single phase system.
(i) A 220V DC series motor draws a current of 20A. The armature resistance is 0.1Ω and series winding resistance is 1.2Ω . Find the back emf.
(j) What are the different types of losses in a transformer? How can these losses be reduced?




PART B

(4 × 10 = 40)

- II. (a) Calculate the current 'I' using Thevenin's equivalent circuit.

(6)

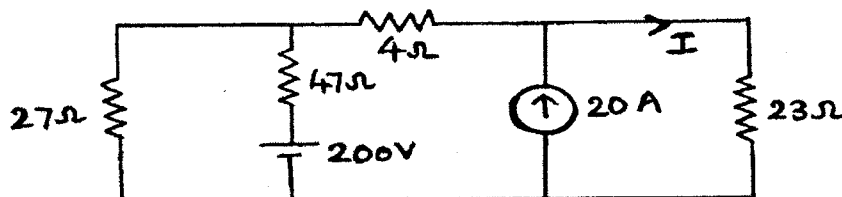


- (b) Two capacitors, A and B, having capacitances of $20 \mu F$ and $30 \mu F$ respectively, are connected in series to a 600 V dc supply. Determine the potential difference across each capacitor. If a third capacitor C is connected in parallel with A and it is then found that the potential difference across B is 400V, calculate the capacitance of C and the energy stored in it.

(4)

OR

(P.T.O.)

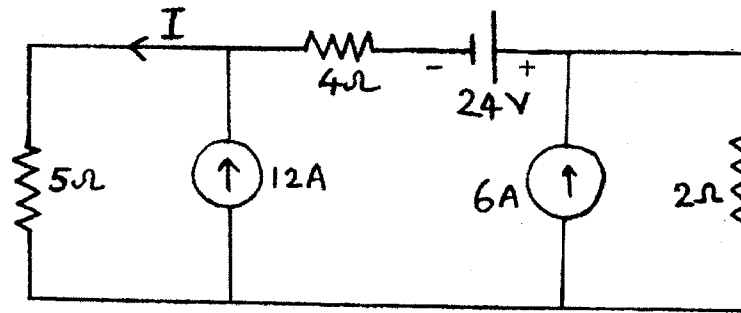- III. (a) State and explain Superposition theorem. (4)
 (b) For the circuit shown, use superposition theorem to calculate the value of current I . (6)



- IV. (a) Explain the working of an energy meter with neat sketches. (6)
 (b) Define mutual inductance in a magnetic circuit. Derive an expression for coefficient of coupling. (4)


OR

- V. (a) Define (i) MMF (ii) Magnetizing force (iii) flux density (iv) reluctance (4)
 (b) A steel ring of 25 cm diameter and of circular cross section 3 cm in diameter has an air gap of 1.5 mm length. It is wound uniformly with 750 turns of wire carrying a current of 2.1 A. Calculate (i) m.m.f. (ii) flux density in air gap (iii) magnetic flux (iv) relative permeability of steel ring. Assume that iron path takes about 35% of total magneto motive force. (6)

- VI. (a) A $10\ \Omega$ resistor and $400\ \mu\text{F}$ capacitor are connected in series to a 240 V sinusoidal ac supply. The circuit current is 5 A. Calculate the supply frequency and phase angle between current and voltage. (4)
 (b) Three inductive coils, each with a resistance of $22\ \Omega$ and an inductance of 0.05 H are connected (i) in star (ii) in delta, to a three phase 415 V, 50 Hz supply. Calculate for each of the above cases (i) phase current and line current (ii) total power absorbed. (6)

OR

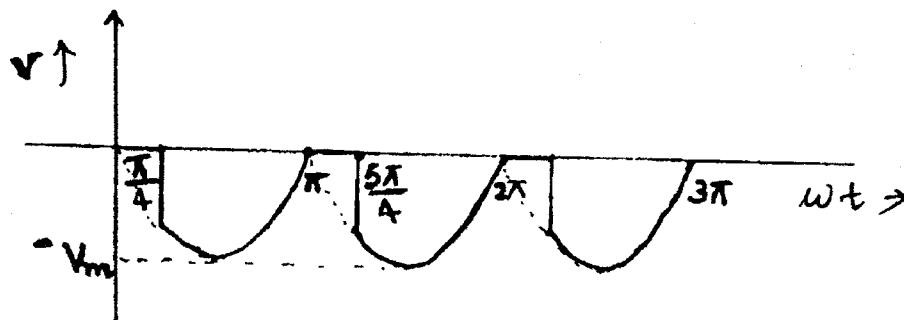- VII. Find the form factor and peak factor of the given altering waveform. (10)



- VIII. With a neat schematic, explain the working of a thermal power plant. (10)

OR

- IX. (a) With a neat sketch explain the constructional details of a DC Machine. (6)
 (b) Derive an equation for back emf in DC motor. (4)
